

## Mini Project 2 Submission

Circuit Design Overview: The circuit design consists of 3 main modules. The first module, called `pwm`, generates the PWM signal, which is then passed through two additional modules to reach the LED, making it appear to dim and brighten. The `pwm` module was copied from Brad Minch's Fade example located here (<https://github.com/bminch/iceBlinkPico>). The inputs to the `pwm` module are provided by the `pwm_wrapper` module that creates the `pwm_value` that is used to control the duty cycle of the PWM signal. The `pwm_wrapper` module allows us to create a PWM signal with an incrementing duty cycle and another PWM signal with a decrementing duty cycle, which we can choose based on the `DUTY_CYCLE_FUNC_MODE` parameter. The top module has the state machine and counter to determine when the state needs to change, and has connections to the LED outputs. In summary, there is the top module that has the state machine and calls on the `pwm_wrapper` module that changes the duty cycle of the PWM signal and then calls on the `pwm` module that actually makes the PWM signal.

System Verilog Files: <https://github.com/H-TejadaDeras/ENGR3410-01.25FA/tree/main/assignments/mini%20project%202>

Demo Video: [https://olincollege-my.sharepoint.com/:v/g/personal/htejada\\_olin\\_edu/EVCPvocJuQRFvVCHf3\\_OascBPYcx5Lxh6NPgMVCMWSq6GA?nav=eyJyZWZlcnJhbEluZm8iOnsicmVmZXJyYWxBcHAIoiJPbmVEcmI2ZUZvckJ1c2luZXNzliwicmVmZXJyYWxBcHBQbGF0Zm9ybSI6IldlYiIsInJlZmVycmFsTW9kZSI6InZpZXciLCJyZWZlcnJhbFZpZXciOiJNeUZpbGVzTGlua0NvcHkifX0&e=kdxkS6](https://olincollege-my.sharepoint.com/:v/g/personal/htejada_olin_edu/EVCPvocJuQRFvVCHf3_OascBPYcx5Lxh6NPgMVCMWSq6GA?nav=eyJyZWZlcnJhbEluZm8iOnsicmVmZXJyYWxBcHAIoiJPbmVEcmI2ZUZvckJ1c2luZXNzliwicmVmZXJyYWxBcHBQbGF0Zm9ybSI6IldlYiIsInJlZmVycmFsTW9kZSI6InZpZXciLCJyZWZlcnJhbFZpZXciOiJNeUZpbGVzTGlua0NvcHkifX0&e=kdxkS6)

State Machine Timing Diagram (next page):

Sample PWM Timing Diagram (next page):



